



L-Università
ta' Malta

MATRICULATION AND SECONDARY EDUCATION CERTIFICATE
EXAMINATIONS BOARD

**SECONDARY EDUCATION CERTIFICATE LEVEL
2025 MAIN SESSION**

SUBJECT:	Engineering Technology
PAPER NUMBER:	Controlled – Unit 2
DATE:	10 th May 2024
TIME:	10:00 a.m. to 11:35 a.m.

**THIS PAPER SHOULD BE RETURNED TO THE INVIGILATOR
AFTER THE EXAMINATION.**

Name of candidate _____

I.D. number _____

School _____

Class _____

Answer **ALL** questions in the space provided.

Scenario

The school teacher at a Technical College will construct and test a number of circuits using different materials and electronic components provided to her by the school technician.

Question 1

K-1 (4 marks)

Based on their electrical characteristics, all materials can be classified into three groups: conductors, semiconductors, and insulators.

a) Categorise the given set of materials into either conductors or insulators, considering their electrical properties. Place them in the appropriate column of Table 1. An illustrative sample from each category is already provided in the table to assist you.

Oil	Porcelain	Copper	Gold
-----	-----------	--------	------

Table 1: Conductors and Insulators

Conductor	Insulator
Aluminium	Glass

(1)

b) Define the term semi-conductor.

(1)

c) The resistance of a copper or aluminium wire is influenced by three different parameters. State any **TWO** of these parameters.

(2)

Question 2

K-3 (4 marks)

- Electrical circuits can be either closed or open.
- Moreover, electrical circuits can be either series, parallel or a combination of the two.

a) Differentiate by highlighting the differences between open and closed circuits.

(1)

b) In the space provided below draw:

- i) A series circuit consisting of a 3 V battery and two resistors of: 1 x 560 Ω and 1 x 680 Ω .

(0.5)

- ii) A parallel circuit made up of a 3 V battery and a 150 Ω resistor in parallel with a 120 Ω resistor.

(0.5)

This question continues on next page.

- c) Figure 1 illustrates a series-parallel circuit.
 From this circuit shown in Figure 1, identify **ONE** series and **ONE** parallel circuit combination by referring to the resistors R1, R2 and R3. Write your answers in the space provided below.

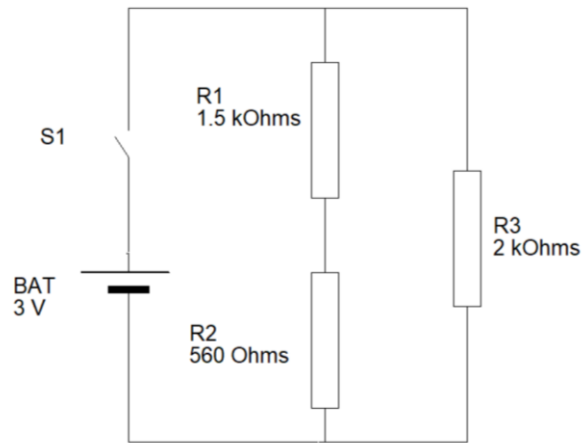


Figure 1: Series-parallel circuit

Series sub-circuit: _____ (1)

Parallel sub-circuit: _____ (1)

Question 3

C-2 (6 marks)

The equivalent resistance of a circuit is important to determine the power supplied by the battery.

- a) Find the total resistance of the circuit shown in Figure 2. Show all your working.

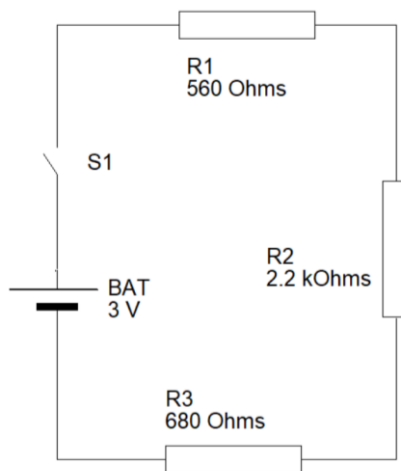


Figure 2: Circuit 1

(2)

b) Find the total resistance of the circuit shown in Figure 3 below. Show all your working.

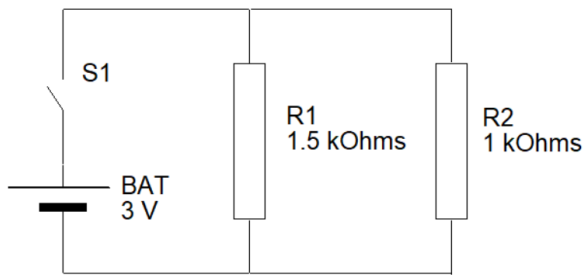


Figure 3: Circuit 2

(2)

This question continues on next page.

Question 4

C-3 (6 marks)

The required equivalent capacitance can be obtained by connecting capacitors in series and/or in parallel in one circuit.

a) Find the total capacitance of the circuit shown in Figure 5 below. Show all your working.

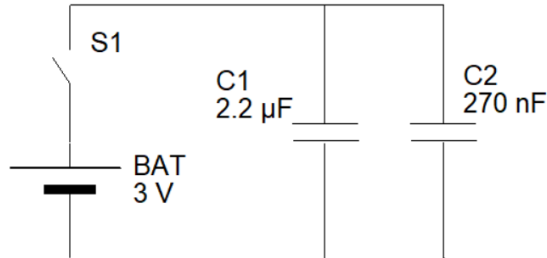


Figure 5: Circuit 4

(2)

b) Find the total capacitance of the circuit shown in Figure 6 below. Show all your working.

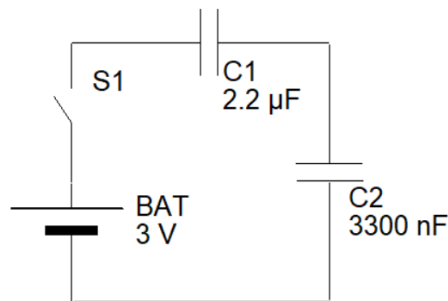


Figure 6: Circuit 5

(2)

This question continues on next page.

- c) Find the capacitance value of capacitor C1 required to obtain a time constant of 2.64 s for the RC circuit shown in Figure 7.

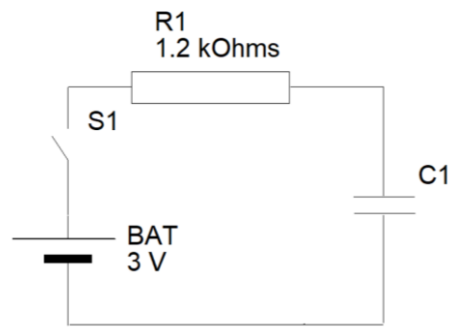


Figure 7: Circuit 6

(2)

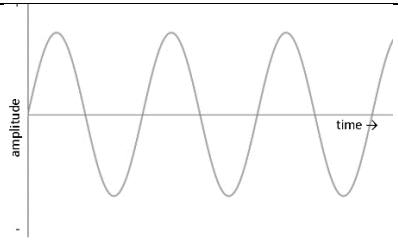

Question 5

K-6 (4 marks)

Different signal waveforms describe the variation of a parameter as a function of time.

a) Identify the **TWO** different signals tabulated in Table 2.

Table 2: Different types of Signals

	Signal	Name
i)		<hr/> <p>(0.5)</p>
ii)		<hr/> <p>(0.5)</p>

(Source: <https://www.seeedstudio.com>)

b) Define **TWO** parameters of a square wave signal, and their SI units.

Parameter 1: _____ (0.25)

SI Unit of Parameter 1: _____ (0.25)

Parameter 2: _____ (0.25)

SI Unit of Parameter 2: _____ (0.25)

This question continues on next page.

c) Label the important features of the oscilloscope shown in Figure 8.

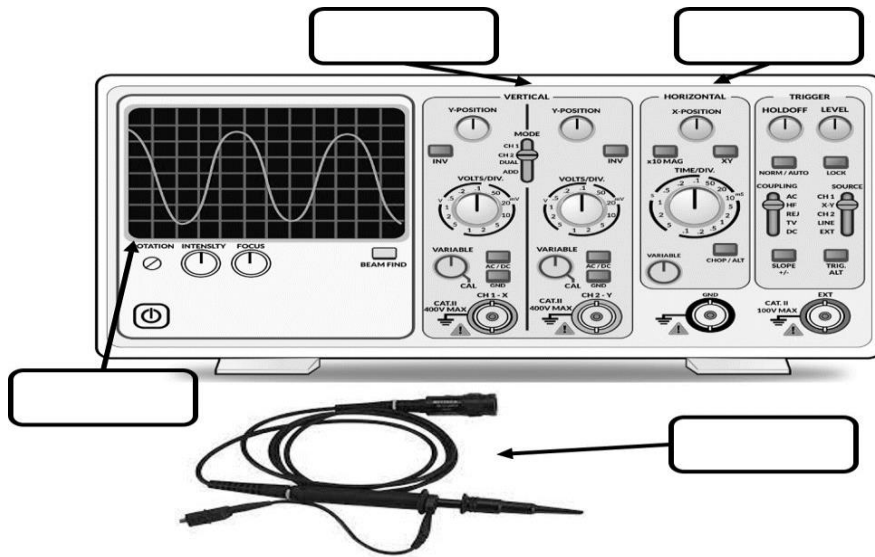


Figure 8: Oscilloscope
(Source: <https://www.electronicshub.org/>)

(2)



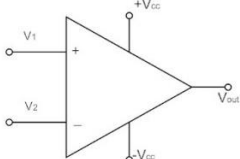

Question 6

K-9 (4 marks)

Different standardised electronic symbols are used to represent different electronic components.

a) Identify all the electronic symbols illustrated in Table 3.

Table 3: Electronic Symbols.

	Electronic Symbol	Name
i)	 (Source: https://www.keystagewiki.com/)	_____ (0.25)
ii)	 (Source: https://www.electrostudy.com)	_____ (0.25)
iii)	 (Source: https://www.electronicshub.org/)	_____ (0.25)
iv)	 (Source: https://www.tutorialspoint.com/)	_____ (0.25)

b) Match the SI units on the left to their respective parameters on the right by connecting a line between them.

Ohms

Current

Farads

Power

Amps

Capacitance

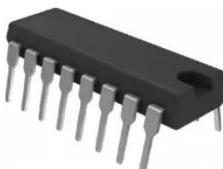
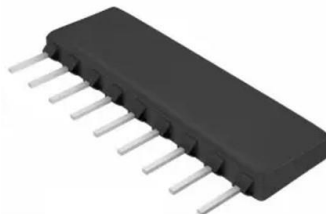


Watts

Resistance

(1)

c) Table 4 below shows different packaging for an operational amplifier and a diode. Identify each of the given package, by underlining the correct answer.

Table 4: Component Packaging.

	Component	Packaging 1	Packaging 2
i)	Operational Amplifier	 Single in line / Dual in Line	 Single in line / Dual in Line
ii)	Diode	 Through hole / Surface mount	 Through hole / Surface mount

(Sources: <https://www.electroschematics.com>, <https://www.electroschematics.com>, <https://eu.mouser.com/>, <https://www.directindustry.com>)

(2)

Please turn the page.



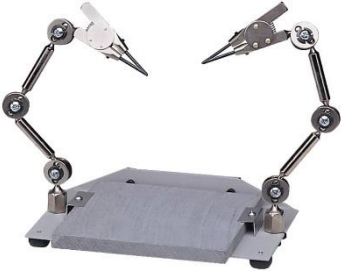

Question 7

K-10 (4 marks)

To construct electronic circuits specialised tools are required.

a) Label the different tools used in the construction of electronic circuits shown in Table 5.

Table 5: Tools

	Tool	Name
i)	 <p>(Source: https://fixit.com.mt/)</p>	<p>_____ (0.25)</p>
ii)	 <p>(Source: https://www.techsoft.co.uk/)</p>	<p>_____ (0.25)</p>
iii)	 <p>(Source: https://grs.com/)</p>	<p>_____ (0.25)</p>
iv)	 <p>(Source: https://dk.farnell.com/)</p>	<p>_____ (0.25)</p>

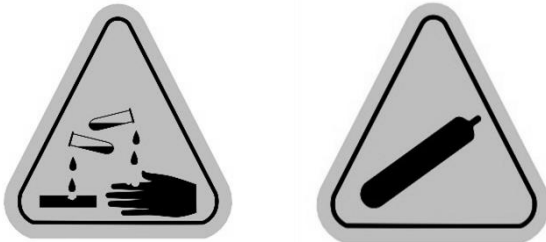

Question 8

C-5 (6 marks)

Different safety precautions need to be taken to mitigate with a number of hazards present during the PCB manufacturing process.

a) Identify the appropriate warning sign for each of the hazardous scenario given in Table 6. Draw a circle around the correct sign.

Table 6: Warning signs for hazardous scenarios.

	Scenario	Warning Sign
i)	A liquid used during the etching process that is highly corrosive	
ii)	A liquid used during the etching process that is flammable	

(Source: <https://www.vectorstock.com/>)

b) Identify **FOUR** hazards that might be present when manufacturing a PCB.

Slipping on the floor Dangerous fumes from solder	Burns Airborne fragments	Chemical spill Falling from heights
--	-----------------------------	--

- Hazard 1: _____ (0.5)
- Hazard 2: _____ (0.5)
- Hazard 3: _____ (0.5)
- Hazard 4: _____ (0.5)

c) Identify **FOUR** ways to eliminate or minimize the risks involved when manufacturing a PCB.

Work in a humid area	Keep the work area safe and clean
Wear appropriate PPE	Work in a well-ventilated area
Use chemicals according to its Data Safety Sheet	Store chemical on shelves

Minimize risk 1: _____ (0.5)

Minimize risk 2: _____ (0.5)

Minimize risk 3: _____ (0.5)

Minimize risk 4: _____ (0.5)

Blank Page